

# DIGITAL LOGIC AND DESIGN PROJECT



WINTER SEMESTER 2016

PROJECT TOPIC:FASTEST  
FINGER FIRST



GROUP MEMBERS:

SHASHANK PATHAK (15BCE1287)

OSHO AGYEYA (15BCE1326)

## AIM:

To design a fastest finger first circuit to find which player pressed the switch first by utilization of basic gates and flip flops made by these gates itself.

## ABSTRACT:

Quiz competitions are held in schools, colleges and also in Television channels as they carry out special programs, various other organizations. The process of identifying a participant whose option button pressed is very critical in timings as they might differ in seconds or milliseconds.


This process of carrying the tedious work is made simple by this Circuit. This Electronic Quiz buzzer enables to identify a particular participant as whom have pressed first amongst all. This Circuit is made up of a simple AND gate IC's and a couple of SR type flip Flop IC's are used in order to set and reset the device. An LED for Each participant is provided such that, it will indicate the person who has pressed the option switch first amongst all and also a beep sound indicator is made available when any switch is pressed. This is made of simple components using an AND gate , Flip Flop IC , LED's and buzzer hence the circuit is cost effective.

---


# COMPONENTS REQUIRED:

- 1) Bread board
  - 2) Wires
  - 3) Switches
  - 4) AND, NAND, NOT, OR gates
  - 5) Battery 9V
  - 6) Winner indicators LED's
  - 7) Buzzer
  - 8) SR Flip Flop using basic gates
  - 9) Resistors 1k ohm
-


# BLOCK DIAGRAM:

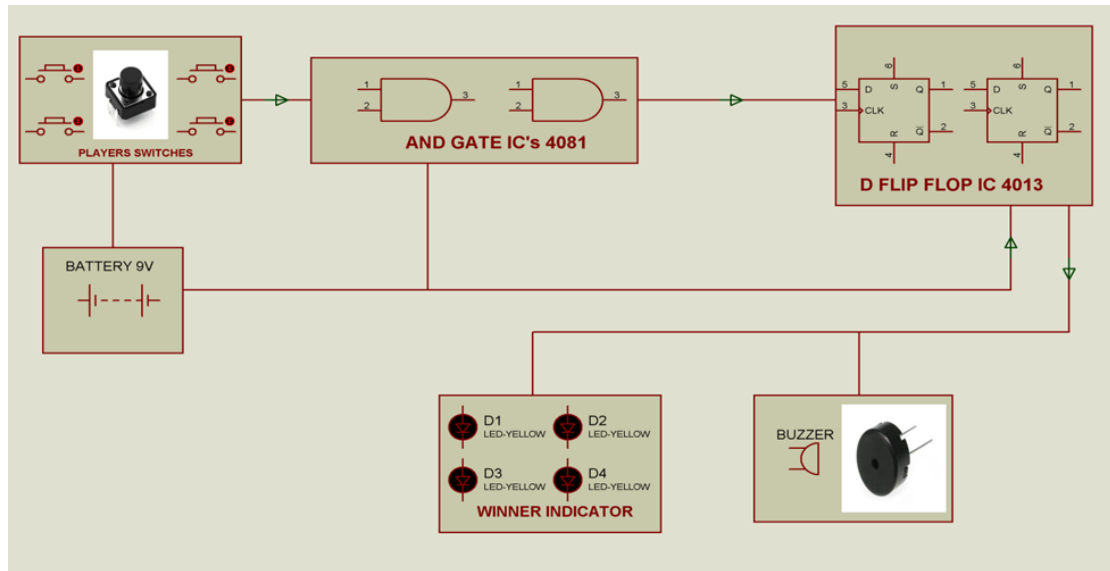


# SR FLIP FLOP BY BASIC GATES

 


(a) internal design

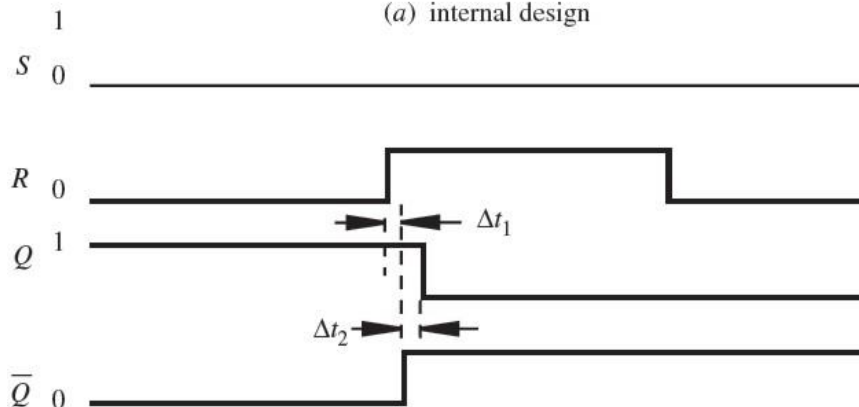

# CIRCUIT DIAGRAM:


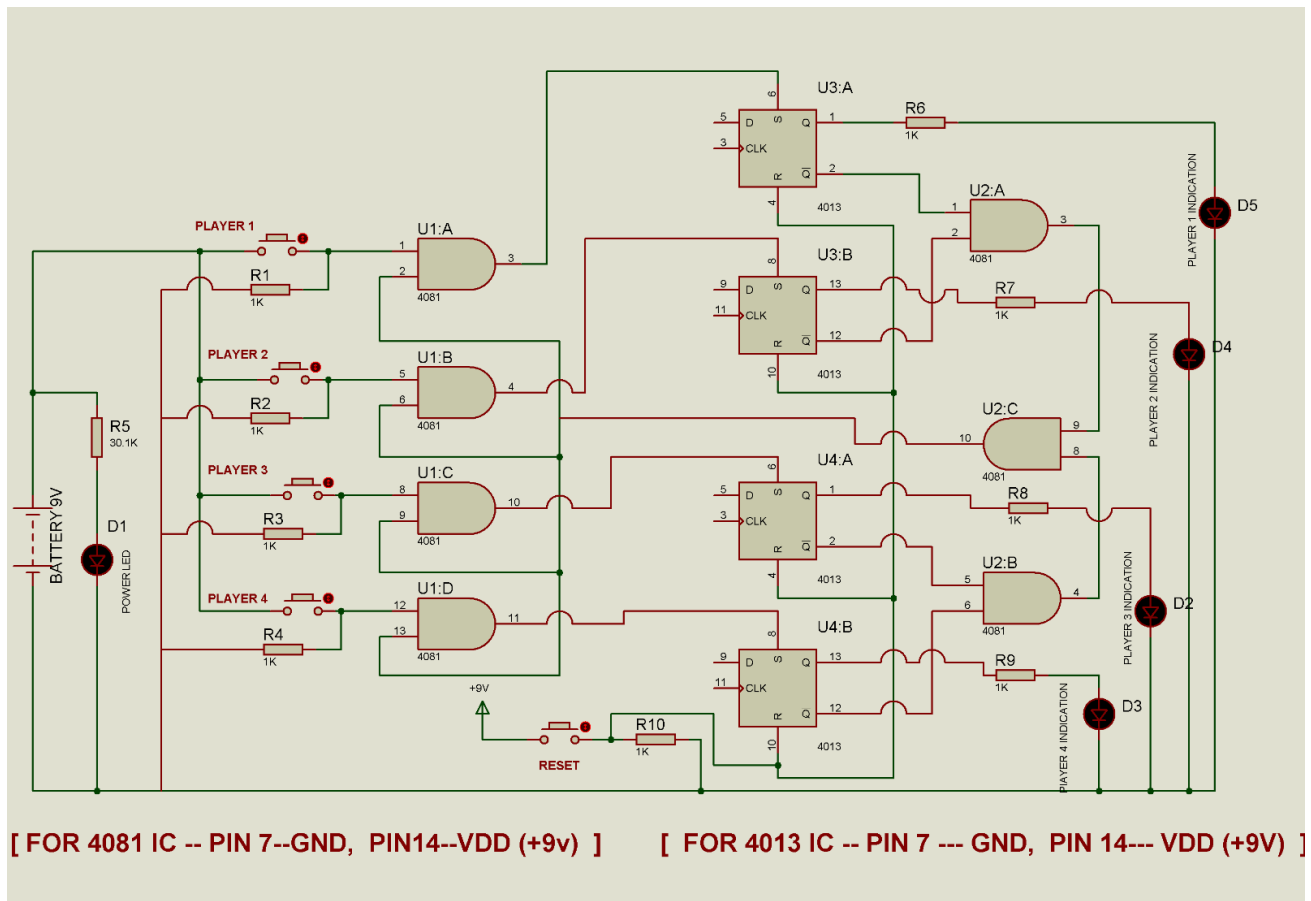


## LTSpice DIAGRAM:


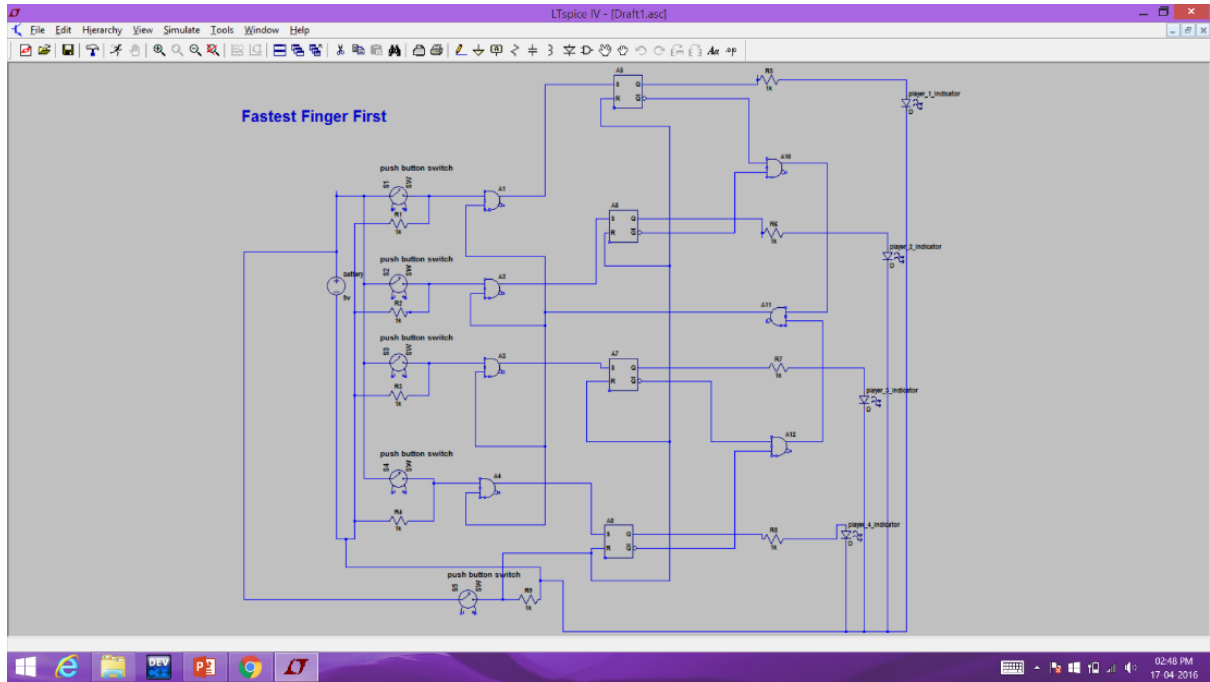





# CIRCUIT UNDER CONSTRUCTION:

  



  

# FINAL PROJECT:

 

## VHDL CODE:

### ->NAND GATE:

```
--import std_logic from the IEEE library
library ieee;
use ieee.std_logic_1164.all;

--ENTITY DECLARATION: name, inputs, outputs
entity nandGate is
    port( A, B : in std_logic;
          F : out std_logic);
end nandGate;

--FUNCTIONAL DESCRIPTION: how the NAND Gate works
architecture func of nandGate is
begin
    F <= A nand B;
end func;
```

## WORKING:

*The working of these codes is as follows:Firstly, the standard libraries are imported. The entity to be declared is NAND gate. The ports signify the input and outputs. Here, A and B are inputs while F is the output. The NAND gate function assigns A nand B to F. The assignment is done according to the respective truth table.*

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

## ->SR FLIP FLOP:

```
library ieee;  
use ieee. std_logic_1164.all;  
use ieee. std_logic_arith.all;  
use ieee. std_logic_unsigned.all;
```

```
entity SR_FF is  
  PORT( S,R,CLOCK: in std_logic;  
        Q, QBAR: out std_logic);  
end SR_FF;
```

Architecture behavioral of SR\_FF is

```
begin  
  PROCESS(CLOCK)  
    variable tmp: std_logic;  
    begin  
      if(CLOCK='1' and CLOCK'EVENT) then  
        if(S='0' and R='0')then  
          tmp:=tmp;  
        elsif(S='1' and R='1')then  
          tmp:='Z';  
        elsif(S='0' and R='1')then  
          tmp:='0';  
        else  
          tmp:='1';  
        end if;  
      end if;  
      Q <= tmp;  
      QBAR <= not tmp;  
    end PROCESS;  
  end behavioral;
```



## WORKING:

*The working of these codes is as follows: Firstly, the standard libraries are imported. The entity to be declared is SR FLIP FLOP. The ports signify the input and outputs. Here, S,R AND CLOCK are inputs while Q AND QBAR are the outputs. The SR flip flop calculates tmp. The calculation is done according to the respective truth table. Finally, tmp is assigned to Q while not tmp is assigned to QBAR.*

<i>S</i>	<i>R</i>	<i>Q</i>
<i>0</i>	<i>0</i>	<i>PREVIOUS STATE</i>
<i>0</i>	<i>1</i>	<i>0</i>
<i>1</i>	<i>0</i>	<i>1</i>
<i>1</i>	<i>1</i>	<i>Z(INVALID)</i>

---

# SIMULATION USING LOGISM:

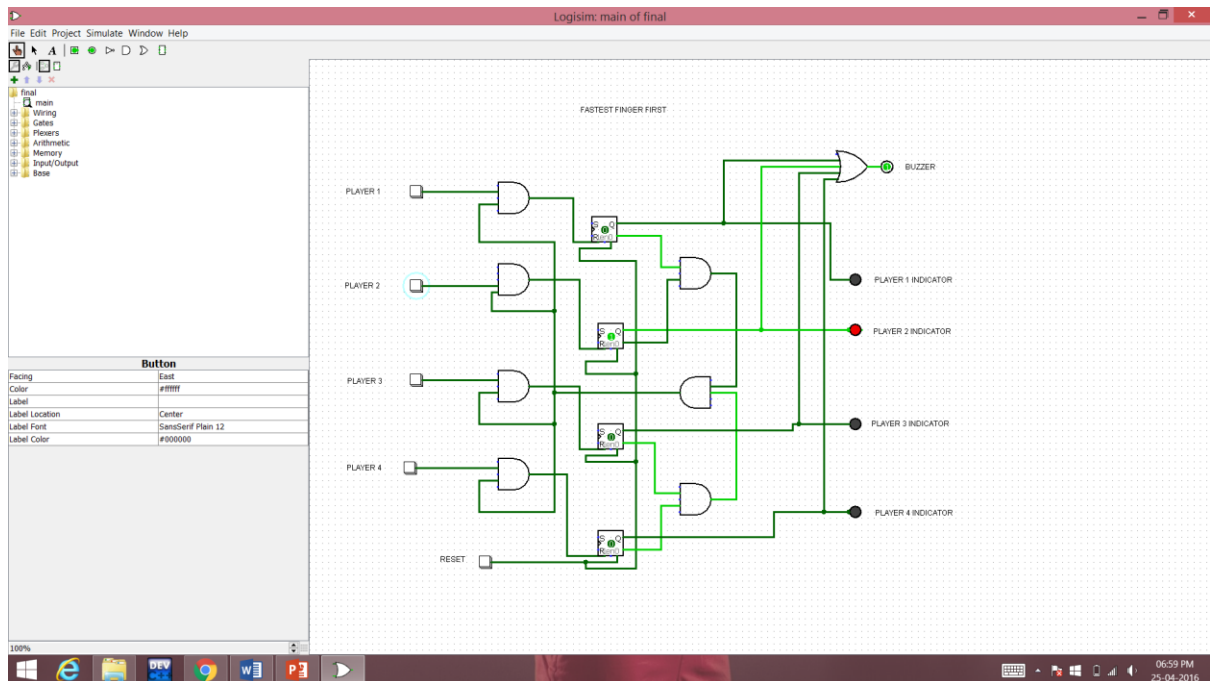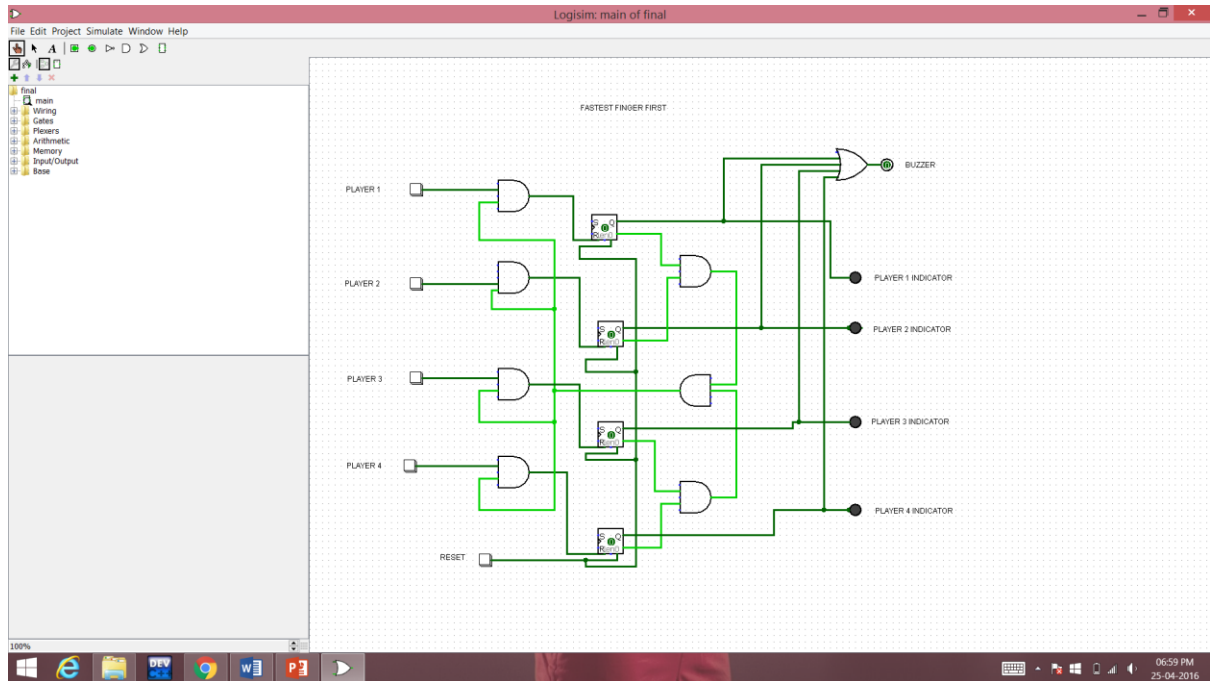





---

---